Circuit construction kit: DC - virtual lab

The student builds a circuit by placing a battery, adding a wire connecting it to a switch, another wire connecting the switch to a light bulb, and another wire connecting the light bulb to the other end of the battery. By closing the switch, current flows and the light bulb turns on.

Instead of a wire, the student discovers that various other conductive objects can be used like a coin, other closed switches, or a paper clip.

Copyright © 2021 The Ontario Educational Communications Authority. All rights reserved.